

# ELECTRIC CIRCUITS

## LESSON 04 RESISTANCE AND $V = IR$

A dimmer switch makes a lamp glow less brightly. What is it actually changing?

### IN THIS LESSON YOU WILL

- describe resistance and its unit, the ohm ( $\Omega$ )
- use  $V = IR$ , including mA and  $k\Omega$
- recognise an ohmic conductor from data or a graph
- explain why heating a metal increases its resistance



NAME

---

CLASS

---

TEACHER

---

TARGET GRADE

---

# HOW THIS BOOKLET WORKS

This is the booklet for **Lesson 4** of the Electric Circuits unit. It builds on the lessons before it; the “Do now” questions and the quick answers at the back help you check what you remember. Keep it: it is your classwork book *and* your revision guide.



## DO NOW

Quick questions from earlier lessons. Remembering again is what makes it stick.



## LEARN IT

The explanation, diagrams and worked examples. Read this again when you revise.



## TRY IT

Practice that builds up: first with support, then on your own.



## LAB

Record measurements from a virtual lab or a required practical.



## EXAM CORNER

An AQA-style question with a tip on how the marks are given.



## REVISE IT

Summary, cover-and-answer questions and an “I can” check to colour in.



**Revising at home?** (1) Read the Learn it pages. (2) Cover them and answer the “Cover the page” questions in Revise it. (3) Check with the quick answers at the back.

## THE ROUTE THROUGH THE UNIT (THIS LESSON IS HIGHLIGHTED)

**01** Complete circuits and symbols

**03** Potential difference

**05** Resistance of a wire RP

**07** Resistors in series and parallel RP

**09** Investigating I–V characteristics RP

**11** Power and energy transfer

**02** Current and charge

**04** Resistance and  $V = IR$

Resistance,  $V = IR$ , ohmic conductors, why heating raises resistance

**06** Series and parallel circuits

**08** I–V graphs

**10** Thermistors, LDRs and sensors

**12** Mains, safety and the National Grid

RESISTANCE AND  $V = IR$ 

AQA Combined 6.2.1.3–6.2.1.4; Physics 4.2.1.3–4.2.1.4; Virtual Lab 3

**BIG QUESTION** A dimmer switch makes a lamp glow less brightly. What is it actually changing?

## BY THE END YOU CAN

- describe resistance and its unit, the ohm ( $\Omega$ )
- use  $V = IR$ , including mA and k $\Omega$
- recognise an ohmic conductor from data or a graph
- explain why heating a metal increases its resistance

resistance

ohm ( $\Omega$ )

ohmic conductor

directly proportional

variable resistor



RETRIEVE

**DO NOW**

From earlier lessons. No notes!

1

What does '6 V across a lamp' mean?


2

Which meter measures p.d., and how is it connected?


3

Two lamps are in series with a 6 V battery. One has 2 V across it. What is across the other?


  
  




EXPLAIN

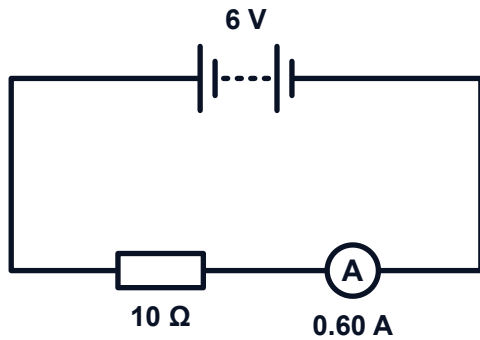**CONTROLLING THE CURRENT**

**Resistance** is how much a component **opposes the current**. For the same p.d., a bigger resistance means a smaller current. Resistance is measured in **ohms ( $\Omega$ )**. A **resistor** has a chosen resistance, such as 10  $\Omega$ , to control the current. A **variable resistor** (the dimmer) lets you change it.



Smaller resistance, bigger current.

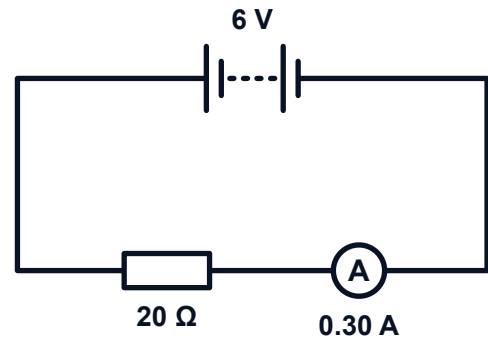


Double the resistance, half the current.

**potential difference = current  $\times$  resistance**

$$V = IR$$

V in volts (V), I in amperes (A), R in ohms ( $\Omega$ )

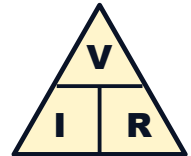Rearranged:  $I = V \div R$  and  $R = V \div I$



#### WORKED EXAMPLE

A resistor has 6.0 V across it and a current of 0.30 A through it. Calculate its resistance.

KNOW       $V = 6.0 \text{ V}$ ,  $I = 0.30 \text{ A}$

EQUATION       $R = V \div I$

SUBSTITUTE  $R = 6.0 \div 0.30$

ANSWER       **$R = 20 \Omega$**

#### YOUR TURN

A lamp has 12 V across it and 0.40 A through it. Calculate its resistance.

KNOW

EQUATION

SUBSTITUTE

ANSWER

#### WORKED EXAMPLE

A 150  $\Omega$  resistor has 3.0 V across it. Calculate the current in milliamperes (mA).

EQUATION       $I = V \div R$

SUBSTITUTE  $I = 3.0 \div 150$

ANSWER       $I = 0.020 \text{ A}$

CONVERT       **$0.020 \times 1000 = 20 \text{ mA}$**

#### YOUR TURN

A 500  $\Omega$  resistor has 2.0 V across it. Calculate the current in mA.

EQUATION

SUBSTITUTE


ANSWER

CONVERT
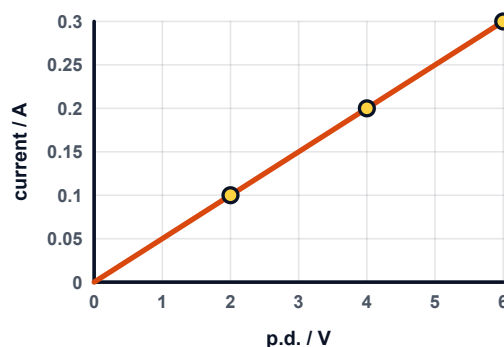
## OHM'S LAW: OHMIC CONDUCTORS


For a **fixed resistor at constant temperature**, the current is **directly proportional** to the p.d.: double the p.d. and the current doubles. The resistance stays the same.

A component like this is an **ohmic conductor**. A graph of current against p.d. is a **straight line through the origin**.



A 20 Ω resistor: straight line through the origin.

## WHY IS THERE RESISTANCE?

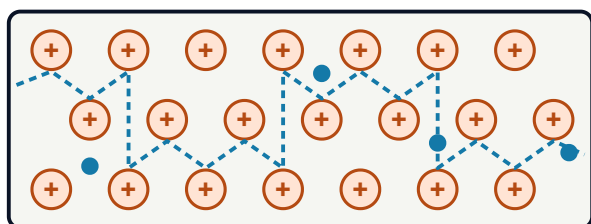

A free electron collides with the ions as it moves through the wire: this is resistance.

Free electrons keep **colliding with the ions** in the metal. This opposes the flow of charge: resistance.

When the metal gets **hotter**, the ions vibrate more, so there are more collisions and the **resistance increases**. That is why Ohm's law needs 'at constant temperature'.



PRACTISE

**TRY IT**

- 1 Two circuits have the same 6 V battery. Circuit A has a 10 Ω resistor; circuit B has a 30 Ω resistor. Tick **one** box.

☐ Circuit A has the bigger current.

☐ Circuit B has the bigger current.

☐ Both have the same current.

☐ You cannot tell.

- 2 **SUPPORTED** Calculate the resistance of a component with 12 V across it and 0.60 A through it.

|            |       |
|------------|-------|
| EQUATION   |       |
| SUBSTITUTE |       |
| ANSWER     | unit: |

- 3 **SUPPORTED** A current of 0.20 A flows through a 15 Ω resistor. Calculate the p.d. across it.

|            |       |
|------------|-------|
| EQUATION   |       |
| SUBSTITUTE |       |
| ANSWER     | unit: |

4

ON YOUR OWN

A  $220\ \Omega$  resistor has  $5.5\ \text{V}$  across it. Calculate the current in mA.


---

---

5

A student measures a component. Complete the table, plot the points and draw a line of best fit.

| p.d. / V | current / A | $V \div I / \Omega$ |
|----------|-------------|---------------------|
| 1.0      | 0.05        |                     |
| 2.0      | 0.10        |                     |
| 3.0      | 0.15        |                     |
| 4.0      | 0.20        |                     |

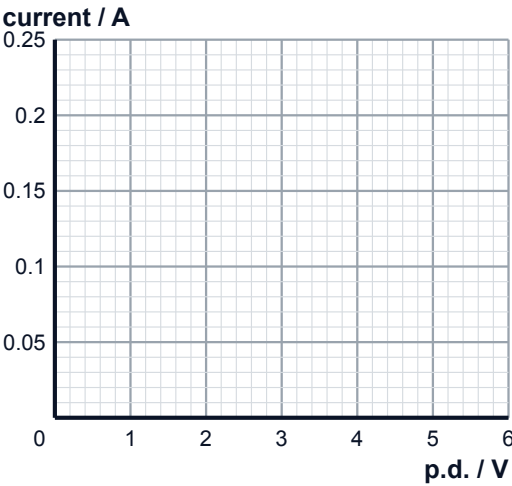

Is the component an ohmic conductor? Use the table and the graph.

---

---

6

Explain why a resistor only has a constant resistance if its temperature stays the same.  
*If the resistor gets hotter, the ions ...*

---

---

---

---

**VIRTUAL LAB 3: DISCOVER THE RESISTANCE RULE**

Set the resistor to **10  $\Omega$** . Change only the battery setting. Measure the p.d. across the resistor and the current.

- 7 Record and calculate.

| Battery setting / V | p.d. / V | current / A | $V \div I / \Omega$ |
|---------------------|----------|-------------|---------------------|
| 2                   |          |             |                     |
| 4                   |          |             |                     |
| 6                   |          |             |                     |
| 8                   |          |             |                     |
| 10                  |          |             |                     |
| 12                  |          |             |                     |

- 8 What happens to the current when the p.d. doubles? What stays constant?

|  |
|--|
|  |
|  |



**Get the marks:** In part (b) use your answer to (a). Quick check:  $3 \times$  the p.d. should give  $3 \times$  the current if  $R$  is constant.

- 9 A fixed resistor has a p.d. of 2.0 V across it and a current of 0.10 A [2 marks]  
through it. Calculate its resistance.

|            |       |
|------------|-------|
| EQUATION   |       |
| SUBSTITUTE |       |
| ANSWER     | unit: |

- 10 The p.d. is increased to 6.0 V. The temperature stays constant. Calculate [2 marks]  
the new current.

|  |
|--|
|  |
|  |

**SUMMARY**

- Resistance opposes the current. Unit: **ohm ( $\Omega$ )**.
- $V = IR$** . Convert mA  $\rightarrow$  A ( $\div 1000$ ) and  $k\Omega \rightarrow \Omega$  ( $\times 1000$ ).
- Ohmic conductor:  $I \propto V$  at constant temperature; the graph is a straight line through the origin.
- Hotter metal  $\rightarrow$  ions vibrate more  $\rightarrow$  more collisions  $\rightarrow$  higher resistance.

**COVER THE PAGE AND ANSWER**

1 What is the unit of resistance?

3 What does an ohmic conductor's I-V graph look like?

2 Write the equation linking p.d., current and resistance.

4 What happens to a metal's resistance as it heats up?

**I CAN...**


describe resistance and state its unit



use  $V = IR$  and its rearrangements



convert mA and  $k\Omega$

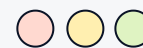

decide from data or a graph whether a component is ohmic



explain why heating increases resistance



# EQUATION TOOLKIT

The equations you have met so far. You will meet these one at a time. Learn each equation **in words** as well as symbols: AQA gives you an equation sheet in the exam (it does not include  $R_{\text{total}} = R_1 + R_2$ ), but knowing the equations by heart makes every question faster.

$$Q = I t$$

Lesson 2

charge flow = current  $\times$  time

C, A, s

Rearranged:  $I = Q \div t$  and  $t = Q \div I$

$$E = Q V$$

Lesson 3

energy transferred = charge  $\times$   
p.d.

J, C, V

Rearranged:  $V = E \div Q$  and  $Q = E \div V$

$$V = I R$$

Lesson 4

p.d. = current  $\times$  resistance

V, A,  $\Omega$

Rearranged:  $I = V \div R$  and  $R = V \div I$

## FOUR STEPS FOR EVERY CALCULATION

**1**

Write down what you know, with units.  
Convert units first  
(minutes  $\rightarrow$  seconds,  
kW  $\rightarrow$  W, mA  $\rightarrow$  A).

**2**

Write the equation you will use, in symbols.

**3**

Substitute the numbers, then rearrange if needed.

**4**




Give the answer with a unit. Ask: is it sensible?

| CONVERT                                                                                       | HOW           | EXAMPLE            |
|-----------------------------------------------------------------------------------------------|---------------|--------------------|
| minutes $\rightarrow$ seconds                                                                 | $\times 60$   | 3.0 min = 180 s    |
| hours $\rightarrow$ seconds                                                                   | $\times 3600$ | 2.0 h = 7200 s     |
| milliamps (mA) $\rightarrow$ amps (A)                                                         | $\div 1000$   | 250 mA = 0.25 A    |
| kilowatts (kW) $\rightarrow$ watts (W); kilohms (k $\Omega$ ) $\rightarrow$ ohms ( $\Omega$ ) | $\times 1000$ | 2.2 kW = 2200 W    |
| kilovolts (kV) $\rightarrow$ volts (V)                                                        | $\times 1000$ | 400 kV = 400 000 V |

## EQUATION TRIANGLES: HELP WITH REARRANGING

- 1 Cover the quantity you want to find.
- 2 The two left **side by side**? **Multiply** them.
- 3 One **above** the other? **Divide** the top by the bottom.

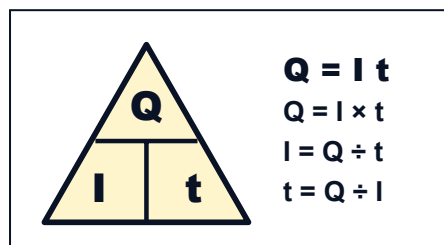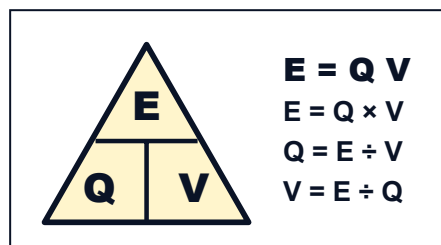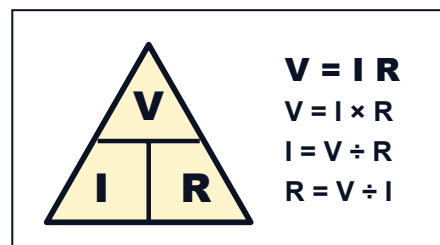Example: to find  $I$  from  $Q = I t$ , cover  $I$ .  $Q$  is above  $t$ , so  $I = Q \div t$ . Triangles only help with rearranging: you still need to learn each equation.



### REFERENCE

## KEY WORDS FROM THIS LESSON

Learn the meaning and spelling. In exams, precise words earn marks: say “p.d. across” and “current through”.

**Directly proportional:** If one quantity doubles, the other doubles. The graph is a straight line through the origin.

**Ohm ( $\Omega$ ):** Unit of resistance.

**Ohmic conductor:** Current is directly proportional to p.d. at constant temperature.

**Resistance ( $R$ ):** How much a component opposes the current. Unit: ohm ( $\Omega$ ).

### CHECK YOURSELF

## QUICK ANSWERS

Answers to the “Do now” and “Cover the page” questions, so you can check yourself when revising. Answers to the longer questions are in your teacher's answer edition.

### DO NOW

1. 6 J of energy is transferred per coulomb.
2. Voltmeter, in parallel (across).
3. 4 V

### COVER THE PAGE

1. Ohm ( $\Omega$ )
2.  $V = I R$
3. A straight line through the origin.
4. It increases.